


Solutions for Energy Harvesting

Examples of charging from Energy Harvesting to LTO battery or Supercap (EDLC)

- Challenges : Supporting various Energy Harvesting : Wireless power transfer (WPT), NFC, solar panels, piezo, etc.
Charge LTO battery or Supercap (EDLC) from unstable/micropower sources

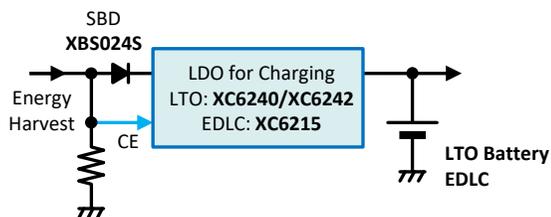Example of 3V~6V input + LTO battery / EDLC


Supported by LTO charging reference circuit



At micro power source

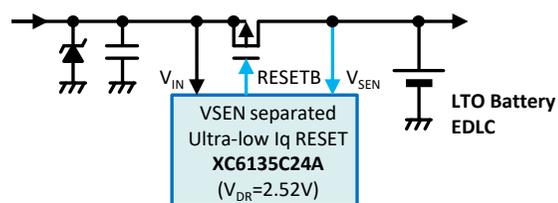
Example of 3V~6V Rectenna and other micro power (a few μ W) + LTO battery / EDLC

ON-OFF control of Pch FET with Ultra-low Iq Voltage Detector




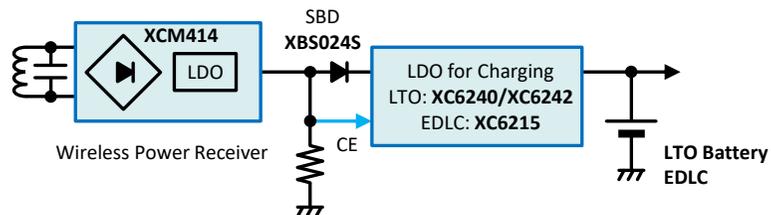Example of Wireless power transfer + LTO battery / EDLC

Charging with wireless power receiving IC + LDO



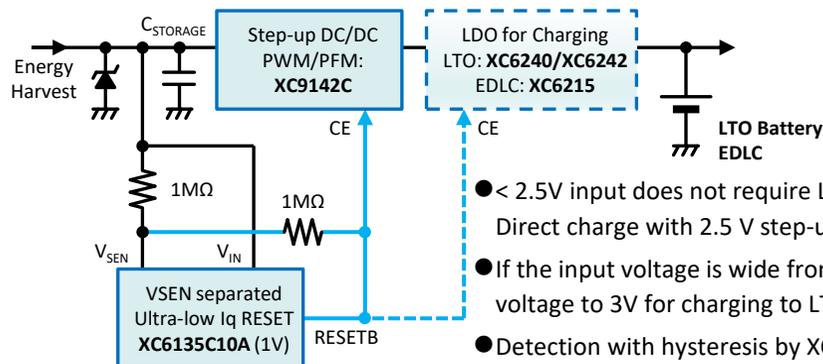Example of 0.9V~2.7V / 0.9V~6V input + LTO battery



- < 2.5V input does not require LDO for charging. Direct charge with 2.5 V step-up output.
- If the input voltage is wide from 0.9 to 6V, boost the voltage to 3V for charging to LTO battery with LDO.
- Detection with hysteresis by XC6135 and resistors. When $C_{STORAGE}$ is charged to 2.1V, the step-up is started to charge, and stopped when it drops to 1V.

For Supercap (EDLC), select the appropriate charge/detect voltages.

- Depending on the voltage characteristics and power of Energy Harvesting, the optimal charging circuit and control voltage varies.

TOREX offers optimal power supply configurations to match the characteristics of your energy harvesting.

Please contact : <https://product.torexsemi.com/en/contact-us/technical-inquiry>